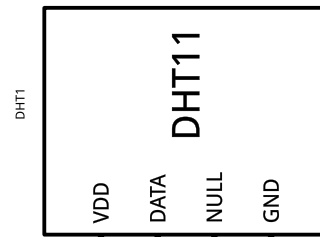


The DHT11 Humidity and Temperature sensor




A photocell(light sensor)



The Serial Robot's circuit Created By: Hamza Boughraira

place your camera
here on the servo

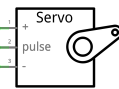

The two H-bridges could
be replaced by the
Arduino's motor shield

